

# SIMCom WCDMA Wireless Module SIM5360 Current Leakage Application Note



<b>Document Title:</b>	SIM5360 Current Leakage Application Note
Version:	0.01
Date:	2013-12-28
Status:	Developing
<b>Document Control ID:</b>	SIM5360_Current_Leakage_Application_Note_V0.01

#### **General Notes**

SIMCom offers this information as a service to its customers, to support application and engineering efforts that use the products designed by SIMCom. The information provided is based upon requirements specifically provided to SIMCom by the customers. SIMCom has not undertaken any independent search for additional relevant information, including any information that may be in the customer's possession. Furthermore, system validation of this product designed by SIMCom within a larger electronic system remains the responsibility of the customer or the customer's system integrator. All specifications supplied herein are subject to change.

#### Copyright

This document contains proprietary technical information which is the property of SIMCom Limited., copying of this document and giving it to others and the using or communication of the contents thereof, are forbidden without express authority. Offenders are liable to the payment of damages. All rights reserved in the event of grant of a patent or the registration of a utility model or design. All specification supplied herein are subject to change without notice at any time.

Copyright © Shanghai SIMCom Wireless Solutions Ltd. 2013



# **Contents**

Contents	 2
Figure Index	 3
Version history	 4
1 Introduction	 5
2 Scope of the document	 5
3 Design guide	5
3.1 UART interface	5
3.2 I <sup>2</sup> C interface	6
3.3 SD interface	6
3.4 RF control	 7
3.5 GPIO	 7
3.6 Power on Indicator	8



# **Figure Index**

Figure 1: Current leakage path	7
Figure 2: UART Circuit (RS232 chip)	8
Figure 3: SD Circuit	8
Figure 4: SD power supply Circuit	9



# **Version history**

Date	Version	<b>Description of change</b>	Author
2013-12-28	0.01	Origin	



## 1 Introduction

User should pay more attention to SIM5360 leakage current. When the module is powered off, the voltage of all digital interfaces (PCM UART, etc) connected with peripheral devices should be less than 0.3V. Otherwise, high level voltages maybe occur in some GPIO pins because of current leakage from above digital interfaces. So if customer uses a GPIO of the module to detect whether the module is turned on or not, there will cause feint.

This document describes how to avoid these problems caused by current leakage.

# 2 Scope of the document

SIM5360 module.

# 3 Design guide

SIMCom recommends some reference design according to the functions of module. These digital interfaces contain PCM, UART, I<sup>2</sup>C, SD and some dedicated GPIOs. Current leakage may occur if there are some defects in user's design.

# 3.1 UART interface

If SIM5360 serial port is used to communicate with PC, a CMOS and RS232 level converter chip is needed. SP3238ECA (provided by Sipex Corporation) is recommended in the reference circuit as below. SP3238ECA can be turned off through the S204 to prevent leakage current.



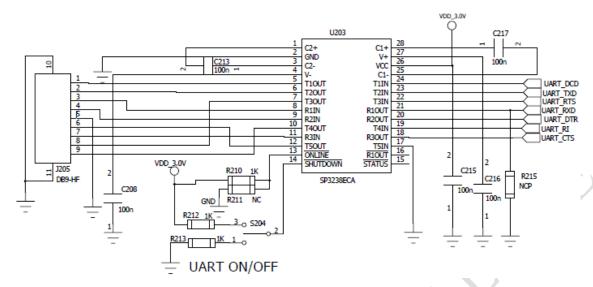


Figure 1: UART Circuit (RS232 chip)

If the serial port communicates with the MCU directly, the UART data lines should not be pulled up by the MCU when module is turned off, otherwise the leakage current will occur.

If UART port is used in Null Modem, UART data lines(except UART\_TXD and UART\_RXD)can be reconfigured as GPIOs. In this case, user must ensure that these data lines can not be pulled up by external device, otherwise the leakage current will occur.

# 3.2 I<sup>2</sup>C interface

I<sup>2</sup>C\_SDA and I<sup>2</sup>C\_SCL of SIM5360 module have been pulled up with two 2.2kR resistors to 2.6V level in module. So user must not pull them up in users' application circuit, otherwise the leakage current may occur.

#### 3.3 SD interface

If some modules provide MMC/SD interface, the VREG\_AUX pin of module is recommended to power the SD card. VREG\_AUX is a 2.85V LDO power output by default, rated for 250mA. The reference circuit is shown as below.



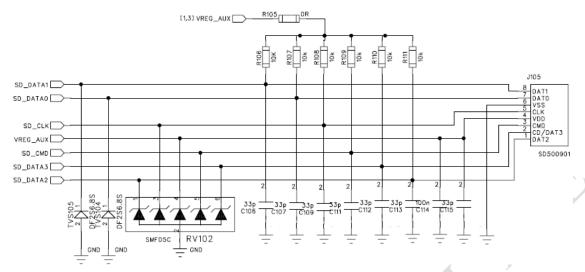


Figure 2: SD Circuit

If an external power supply is used for SD card, VREG\_AUX is also recommended to enable the power supply. The reference circuit is shown as below.

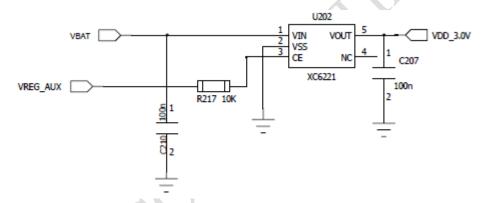


Figure 3: SD power supply Circuit

If module SD interface is pulled up by external power in Figure 3 or by VDD\_3.0V from the above U202 but which is enabled by external level, leakage current may occur.

#### 3.4 RF control

GPIO4 of SIM5360 module is configured to enable or disable flight mode by default. GPIO4 has been pulled up to 2.6V level in module. So user must not pull them up in users' application circuit, otherwise current leakage may occur.

#### **3.5 GPIO**

There are some GPIOs reserved by SIMCom module for user's application circuit. Module can communicate with host or other processor by these GPIOs. Use them correctly can prevent current leakage occurrence. If a GPIO is configured as input, current leakage may occur if user pulls them up in application circuit. So it is not needed to pull them up.



## 3.6 Power on Indicator

Because of current leakage, if some dedicated GPIO is used as the module power on indication, an error detection may generate. We recommend use the VREG\_AUX pin of the module as a power-on indicator. VREG\_AUX is a 2.8V LDO when module is in power-on status, and 0V when it is in power-off status. So it can well be used for module power on/off indication. The reference circuit is shown as below.

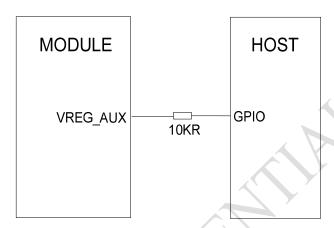


Figure 4: Power on Indicator



## **Contact us:**

# Shanghai SIMCom Wireless Solutions Ltd.

Add: Building A, SIM Technology Building, No.633, Jinzhong Road, Changning District,

Shanghai, P. R. China 200335

Tel: +86 21 3252 3300 Fax: +86 21 3252 3301 URL: <u>www.sim.com/wm</u>