

MBI5001/5016

Constant Current LED Driver

Why is a Constant Current LED Driver necessary?

When using LEDs in display panels like monochromatic, scrolling message board, or a full color video display, LEDs must share consistent characteristics with respect to brightness to avoid the quilted, patchwork appearance. Proper brightness binning of LEDs is critical to the fabrication of a quality LED display.

The nature of the LED manufacturing process often dominates that the LED manufacturers must ship several brightness bins to satisfy users' demands. Even if a given shipment may be satisfied with a single brightness bin, it could be of no guaranty that the next shipment may be of the same brightness bin. This situation is typical of discrete LED devices, LED numeric displays and LED dot matrix blocks.

Understanding the nature of LEDs, the same current flowing through a class of LEDs will result the same brightness, with very limited variation. To light LEDs with the same brightness, users shall maintain the same current flowing through the class of LEDs. That is why a Constant Current driver is needed.

What is a Constant Current Driver?

A Constant Current driver is an integrated circuit device designed specifically to work with LEDs in sign and display applications. Through the use of user-settable, constant current outputs, the Constant Current driver regulates the current through LED loads independent of external factors, such as variations in LED Vf, power supply drift, etc. Once a current value is set, the LED driver will continually track that current regardless of the factors mentioned earlier. A unique, integral feedback mechanism actually monitors the current flow in a given LED or string of LEDs and dynamically adjusts the output to maintain the programmed current level.

How do Constant Current Drivers, MBI5001 and MBI5016, Work?

The Constant Current output stage is an open-drain driver array, which employs an innovative, dynamic, and current regulating scheme. A single resistor tied from MBI5001or MBI5016 to ground sets the desired current (see Fig. 1). Each output of the open-drain array will drive a single LED or series/parallel combinations of LEDs, maintain the desired current on each output string (see Fig. 2 and 3) and typically eliminate the requirement for a current limiting resistor in each string. Each output is equalized to deliver the same current level, even with various LED loads.

The Constant Current driver actually incorporates several of the functions necessary for the control of LEDs in a dynamic variable message sign application. In addition to the constant current output feature, the device family also addresses the decoding and setup functions by incorporating built-in shift register and latch stages. Serial data, sent directly to the driver, is decoded and latched to the constant current outputs, setting up the desired output sequence.



Fig. 1



Fig. 2

Cascading a String of MBI5001 or MBI5016

All image data could be commanded and shifted from a single source (see Fig. 2). MBI5001 and MBI5016 preserve a data setup time and data hold time to ensure the data shift firmly among the ICs. The wiring delay of the signal of CLK should be matched by the wiring delay of the signal of SDO. The successive MBI5001 and MBI5016 thus receive the correct image data.



Fig. 3

Selections of Rext (Current-setting Resistor)

The value of the resistor, R_{ext} , determines the current that the outputs of a constant current driver will maintain. A resistor R_{ext} becomes a part of a reference circuit and results a reference current, Iref, which is mapped to each output of the device.

 R_{ext} is selected from the graph R_{ext} - lout (see Fig. 4, an example of MBI5001) which is included in the device shipment. To determine the value of R_{ext} , the desired current value (lout) must first be located along the vertical axis of the graph. This point is then transferred horizontally to the intercept point on the curve. The corresponding point on the horizontal axis of the graph will yield the value of R_{ext} required to program the device for the desired current.





The effective R_{ext} is the total resistance perceived from Pin 23, R-EXT, to Pin 1, GND.



Fig. 5 The current, lout, shown in the graph R_{ext} - lout is obtained when Vout = 0.8V.

In a panel application, several MBI5016 ICs are individually controlled by separate resistors and are commonly controlled by a trimming resistor. The following is the case for four MBI5016 sharing a common Rtrim.



Fig. 6

The Effective R_{ext} will be Rext0 + 4 x Rtrim, considering a single MBI5016 case. The following table is a comparison for single R_{ext} and Rext0 with Rtrim when obtaining the same current.

R _{ext} t for a single MBI5016	Output Current, lout, measured with	Rtrim is tuned to obtain the same lout when Rext0	Effective R _{ext}
	load		
4297 Ω	10 mA	Rtrim = 789 Ω	1.3K + 4 x 789 = 4456
3240 Ω	12. 96 mA	504 Ω	1.3K + 4 x 504 = 3316
2760 Ω	15 mA	381 Ω	1.3K + 4 x 381 = 2824
2265 Ω	18 mA	249 Ω	1.3K + 4 x 249 = 2296
2009 Ω	20 mA	181 Ω	1.3K + 4 x 181 = 2024
1805 Ω	22 mA	126 Ω	1.3K + 4 x 126 = 1804

The Effective R_{ext} to obtain the same lout is very close to R_{ext} for a single MBI5016. The above experimental data are randomly selected from our inventory. The summary is thus popular and conclusive.

Likewise, when 8 MBI5016 ICs are connected to share a single Rtrim, the multiplication should be 8 instead of 4.

R _{ext} for a single MBI5016	Output Current, lout, measured with customer's LED load	Rtrim is tuned to obtain the same lout when Rext0 is fixed at $1.3 \text{ K}\Omega$.	Effective R _{ext}
4297 Ω	10 mA	Rtrim = 394 Ω	1.3K + 8 x 394 = 4452
3240 Ω	12. 96 mA	252 Ω	1.3K + 8 x 252 = 3316
2760 Ω	15 mA	190 Ω	1.3K + 8 x 190 = 2820
2265 Ω	18 mA	124 Ω	1.3K + 8 x 124 = 2292
2009 Ω	20 mA	90 Ω	1.3K + 8 x 90 = 2020
1805 Ω	22 mA	63 Ω	1.3K + 8 x 63 = 1804

If $R_{ext} = 1805 \Omega$ could result lout = 22 mA for a single MBI5016, Rtrim = 63 Ω (shared by 8 MBI5016) plus individual $R_{ext}0 = 1.3 \text{ K}\Omega$ will also result lout= 22 mA. Rtrim = 63 Ω is obtained by (R_{ext} (1805 Ω) - 1.3 K Ω)/8 = 63 Ω .

The customer could still use the equation to obtain the Rtrim = $(\text{Rext} - 1.3 \text{ K}\Omega)/8$.

The Rtrim does not consider the serial resistance on customer's application board. There will be slight modification when concerning the serial resistance.

Selections of the LED Voltage Supply

A constant current driver regulates the current flow through LEDs by effectively absorbing the excess voltage as required to maintain the programmed current level.

The LED power supply voltage is determined by the following formula:

VLED (total supply voltage) = Vf LED + \triangle Vf LED + VCE,

where

Vf LED = minimum forward voltage of LEDs,

 $\Delta\,Vf$ ${\mbox{\tiny LED}}$ = the maximum deviation of Vf ${\mbox{\tiny LED}}$ in the LED class, and

VCE = voltage drop from the driver output to ground.

V $_{\text{LED}}$ must be selected high enough so that V_CE $\geq 0.8V$ to maintain the constant current invariant to Δ Vf $_{\text{LED}}$.

Power Dissipation Considerations

The power dissipation may be minimized by selecting an adequate LED voltage supply.

The anticipated power dissipation of the device may be calculated by the following formula:

PD1 = # outputs x lout(ave) x (VoL + \triangle Vf LED)+ VDD x IDD,

where

outputs = the number of outputs of the device,

lout(ave) = the average output current,

VoL = voltage drop from the driver output to ground,

V_{DD} = logic supply voltage, and

IDD = device logic supply current.

Excess V_{LED} will cause excess V_{OL} and thus excess power dissipation.

lout(ave) = the average output current = lout (set by Rext) x Duty Cycle (set by /OE).

Considering the package limitation, it is important to know the $R_{th(j-a)}$ values of different kinds of package. Suppose, allowing Tj (max) = 150 °C (max. junction temperature), then the maximum power dissipation capability PD2,

PD2 (at Ta = 0X°C) = (150°C – X°C) / R_{th(j-a)} ------ <1>

When in thermal equilibrium at room temperature, PD1 =< PD2 (at Ta = 25° C).

Model	PD _{max,} @ Ta =25°C	R _{th(j-a)}	PD _{max,} @ Ta =85°C
MBI5001CN (DIP)	1.64 W (on PCB)	76 °C/W, Ta = 25°C	0.85 W (on PCB)
MBI5001CD (SOP)	1.06 W (on PCB)	117 °C/W, Ta = 25°C	0.54 W (on PCB)
MBI5001CP (SSOP)	0.88 W (on PCB)	141 °C/W, Ta = 25°C	0.45W (on PCB)
MBI5016CNS (DIP)	1.52 W (on PCB)	82 °C/W, Ta = 25°C	0.79 W (on PCB)
MBI5016CF (SOP)	1.30 W (on PCB)	96 °C/W, Ta = 25°C	0.67 W (on PCB)
MBI5016CP (SSOP)	1.11 W (on PCB)	112 °C/W, Ta = 25°C	0.57 W (on PCB)

Macroblock's LED Drivers

PD_{max}, @ Ta =25°C is calculated from equation <1>.

Application Brief-Printed Circuit Board- Layout Considerations

The constant current drivers utilize one pin for both logic ground and power ground. Care should be taken to minimize inductance and impedance within the ground pattern to avoid switching-noise induced erroneous operation. The Rtrim does not consider the serial resistance on customer's application board. There will be slight modification when concerning the serial resistance.